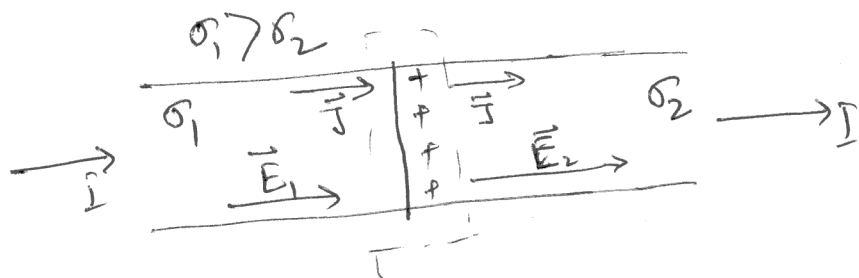


Assignment 5 (Sols.)

1.



Normal component of \vec{J} same on left & right of junction.

$$\therefore |\vec{E}_1| = \frac{J}{\sigma_1}, \quad |\vec{E}_2| = \frac{J}{\sigma_2} \quad (\because \sigma_1 > \sigma_2 \therefore E_2 > E_1).$$

By Gauss's law, the difference in the electric fields gives the surface charge density, σ' as,

$$E_2 - E_1 = \frac{\sigma'}{\epsilon_0}$$

$$\Rightarrow \frac{J}{\sigma_2} - \frac{J}{\sigma_1} = \frac{\sigma'}{\epsilon_0} \Rightarrow \sigma' = \frac{J\epsilon_0}{\sigma_2} \left(\frac{1}{\sigma_2} - \frac{1}{\sigma_1} \right).$$


If A is the area of the interface, then,

$$Q = \sigma' A \quad \& \quad I = JA = \frac{JQ}{\sigma'}.$$

$$\therefore Q = \frac{I\sigma'}{J} = \frac{I}{J} \cdot \frac{J\epsilon_0}{\sigma_2} \left(\frac{1}{\sigma_2} - \frac{1}{\sigma_1} \right)$$

$$\therefore \boxed{Q = \frac{I}{J} \epsilon_0 \left(\frac{1}{\sigma_2} - \frac{1}{\sigma_1} \right)}$$

3.

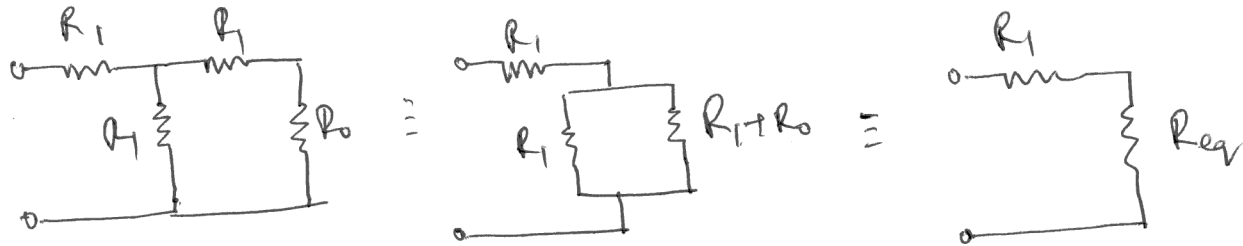

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_1 + R_0}} = \frac{R_1 (R_1 + R_0)}{R_1 + (R_1 + R_0)}$$

$$\text{Finally, } R = R_1 + R_{eq} = R_1 + \frac{R_1 (R_1 + R_0)}{R_1 + R_1 + R_0}$$

We require, $R = R_0$.



$$\therefore R_0 = R_1 + \frac{R_1(R_1 + R_0)}{2R_1 + R_0} \Rightarrow \frac{R_1(2R_1 + R_0) + R_1(R_1 + R_0)}{2R_1 + R_0}$$

$$\Rightarrow R_0(2R_1 + R_0) = R_1(2R_1 + R_0 + R_1 + R_0) = R_1(3R_1 + 2R_0)$$

$$\Rightarrow 2R_0R_1 + R_0^2 = 3R_1^2 + 2R_0R_1 \Rightarrow R_0^2 = 3R_1^2$$

$$\therefore \boxed{R_1 = \frac{R_0}{\sqrt{3}}}$$

4.

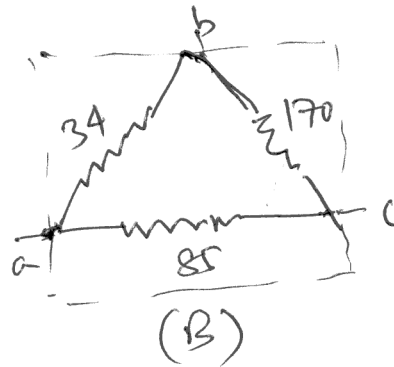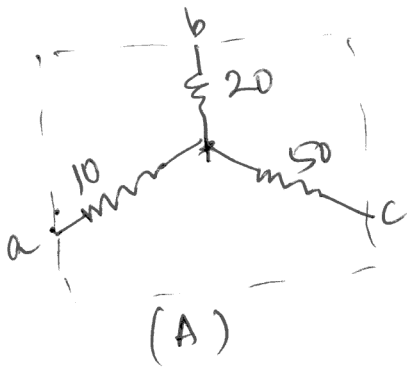

For (A), resistance between any 2 terminals ~~is~~ is basically the series combo of the 2 resistors which connect the terminals. The third resistance does not feature. Therefore, the resistance between terminals (a) & (b) would be,

$$R_{ab}^A = (10 + 20)_1 \Omega = 30 \Omega.$$

For (B), resistance between 2 terminals would involve a resistor in || with 2 others being in series.

For example, to find the resistance between terminals (a) & (b), 34Ω is in || to the

series combination of 170Ω and 85Ω .


$$\therefore R_{AB}^B = \left(\frac{1}{\frac{1}{34} + \frac{1}{170+85}} \right) \Omega = \frac{1}{\frac{255+34}{34 \times 255}}$$

$$= \frac{15 \times 255 \times 34}{289} \Omega = 30\Omega = R_{AB}^A$$

You can similarly show for the other 2.

These are the only 2 possible configurations.

5.

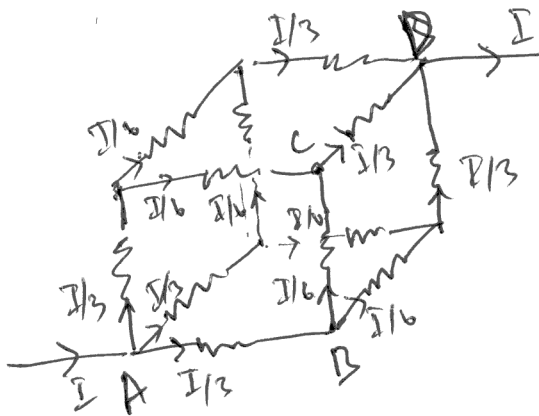

Resistors at the edges of the cube all have same value R_0 .
A current I entering at A will get equally divided in the three sides and so on.


Now take any path say ABCD & for that path,

$$V_{AD} = \underbrace{\frac{I}{3} R_0}_{AB} + \underbrace{\frac{I}{6} R_0}_{BC} + \underbrace{\frac{I}{3} R_0}_{CD} = \frac{5}{6} R_0 I$$


$$\therefore \boxed{R_{AD} = \frac{V_{AD}}{I} = \frac{5}{6} R_0}$$

less than and greater than R ?


[2.5]

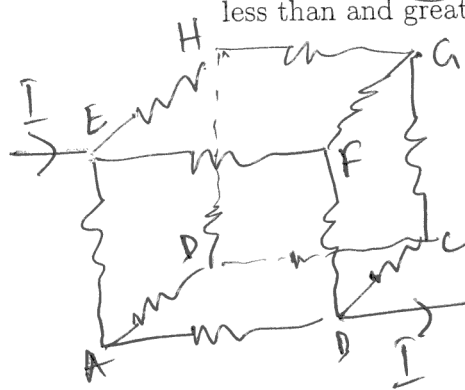

==

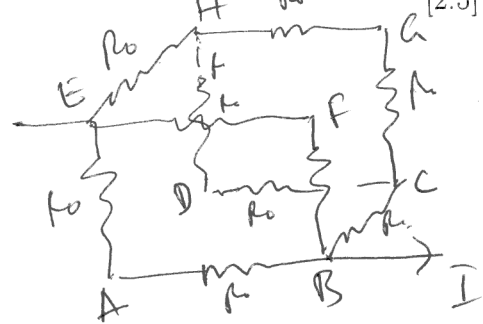

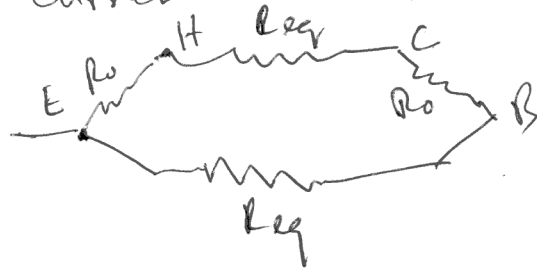
By symmetry, A & F & D & G are equivalent.
Current in the branches AD & FC must be zero.



$$\frac{1}{R_{eq}} = \frac{1}{R_0 + R_1} + \frac{1}{R_0 + R_1}$$

$$= \frac{1}{R_1}$$

$$\therefore R_{eq} = R_1$$

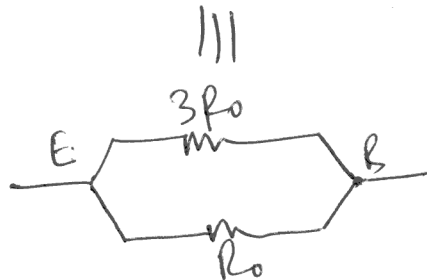

$$\therefore R_{EB} = \frac{1}{\frac{1}{3R_0} + \frac{1}{R_1}} = \frac{3}{4} R_0$$