



# IDC102: Hands-on Electronics

## Lecture - 5

**Inductors**

IISER



IISER

*Satyajit Jena, 06/06/2022*

*ସତ୍ୟଜିତ ଜେନା, ୦୬/୦୬/୨୦୨୨*

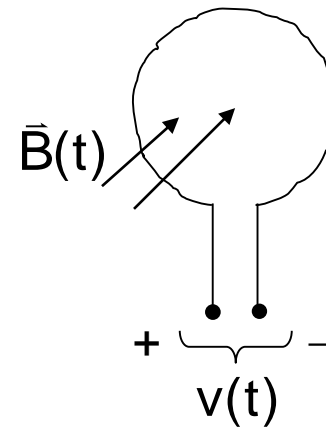
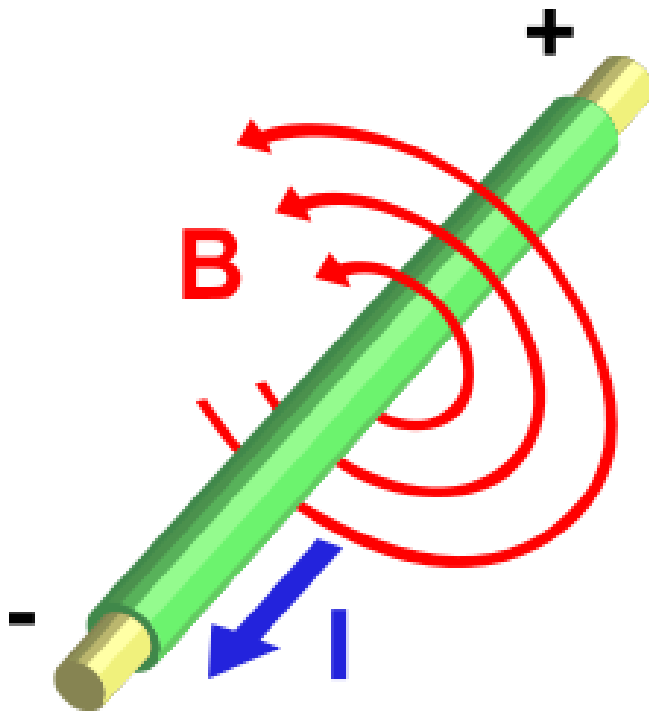
# Induction



- The flow of current induces a magnetic field (Ampere's Law)
- A change in magnetic field through a loop of wire induces a voltage (Faraday's Law)


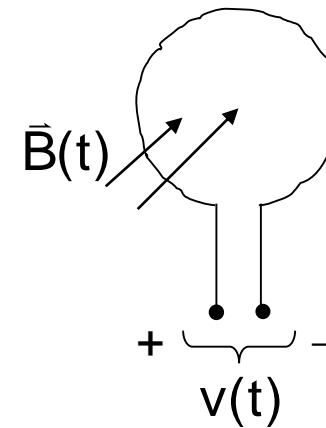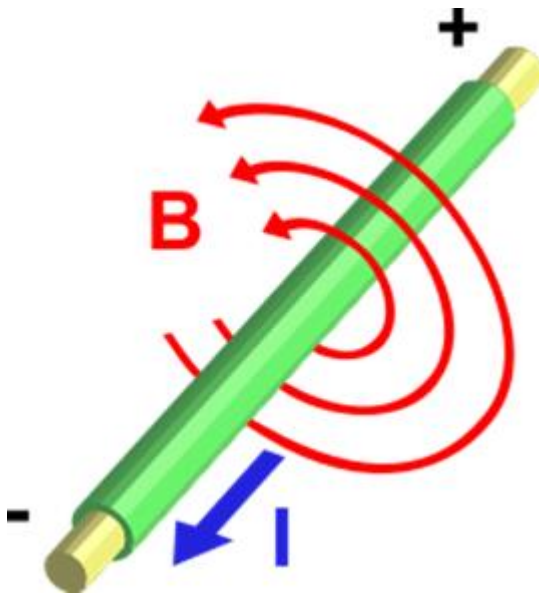
# Induction


- When we connect a voltage source to a wire, current clearly takes a little time to get moving
- Thus, the magnetic field builds to some maximum strength over time



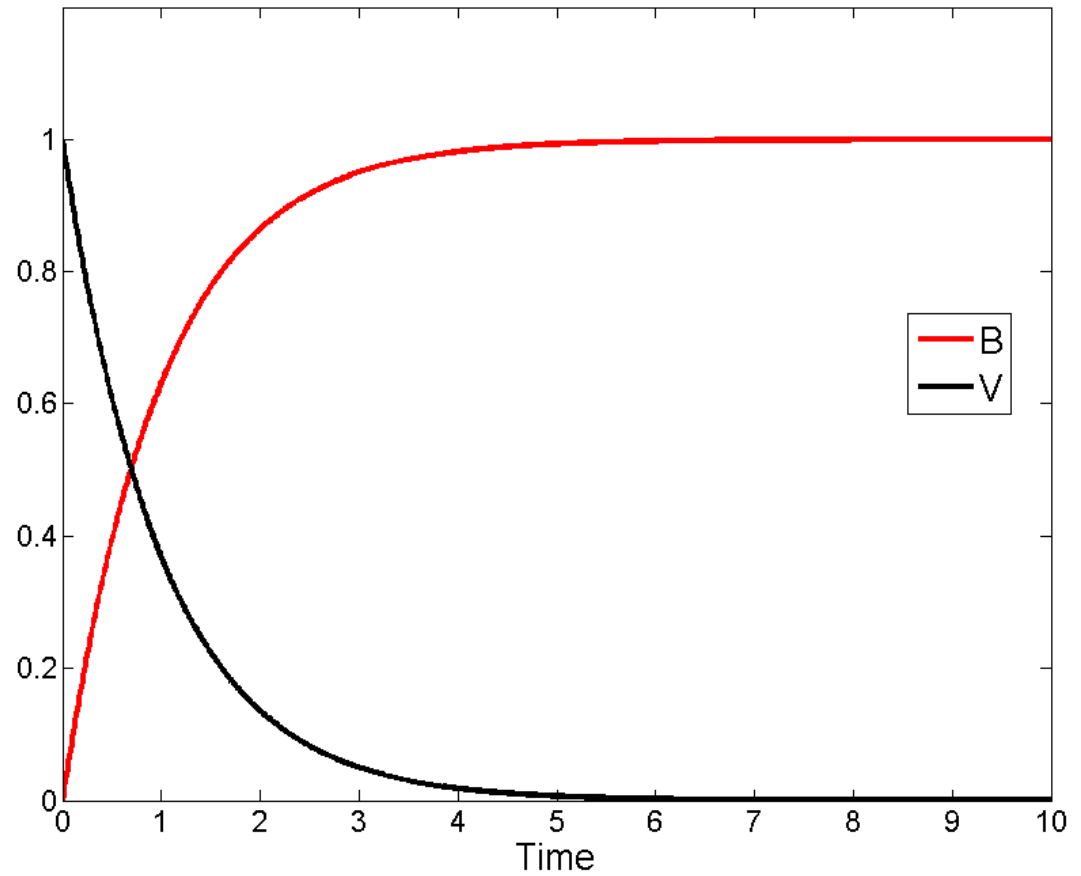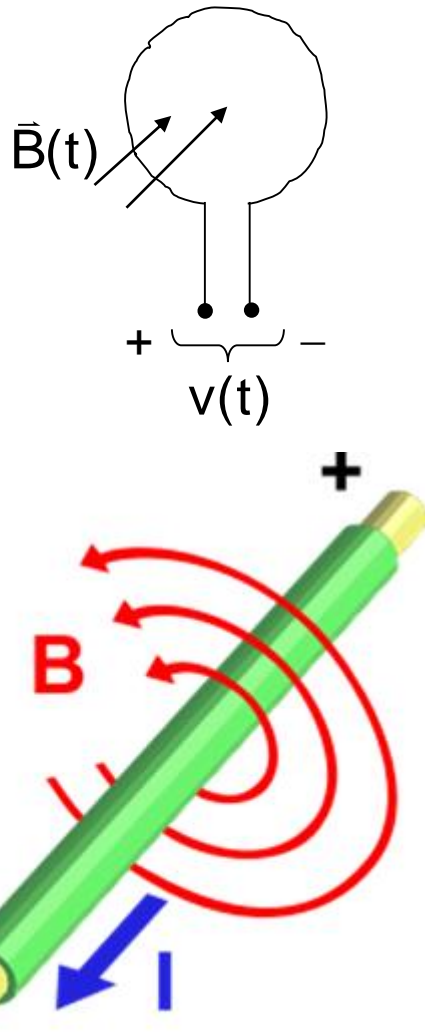


Current in a wire ~~causes~~ induces a voltage in any nearby circuit

- Two fundamental principles of electromagnetics:
  1. Moving electrons create a magnetic field
  2. Change in a magnetic field causes electrons to move... it induces a current
- An inductor is a coil of wire through which electrons move, and energy is stored in the resulting magnetic field
- Stores energy in an magnetic field created by the electric current flowing through it.
  - Inductor opposes change in current flowing through it.
  - Current through an inductor is continuous; voltage can be discontinuous.

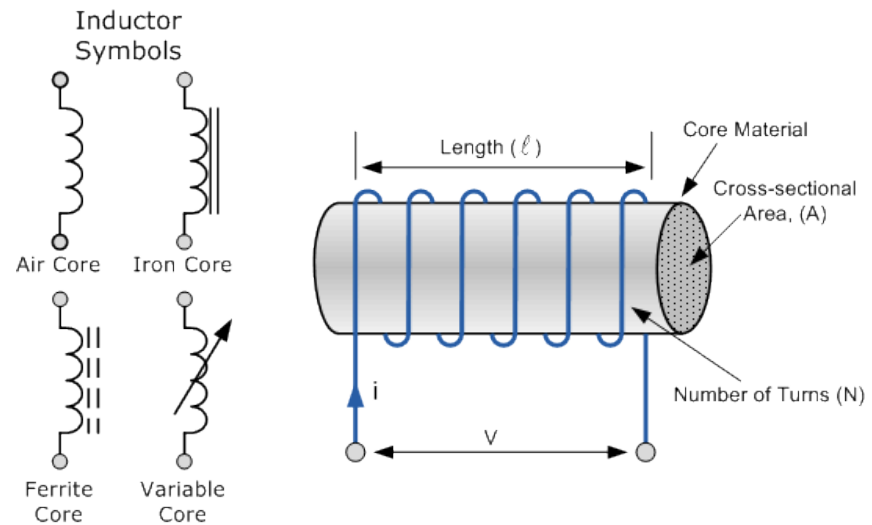


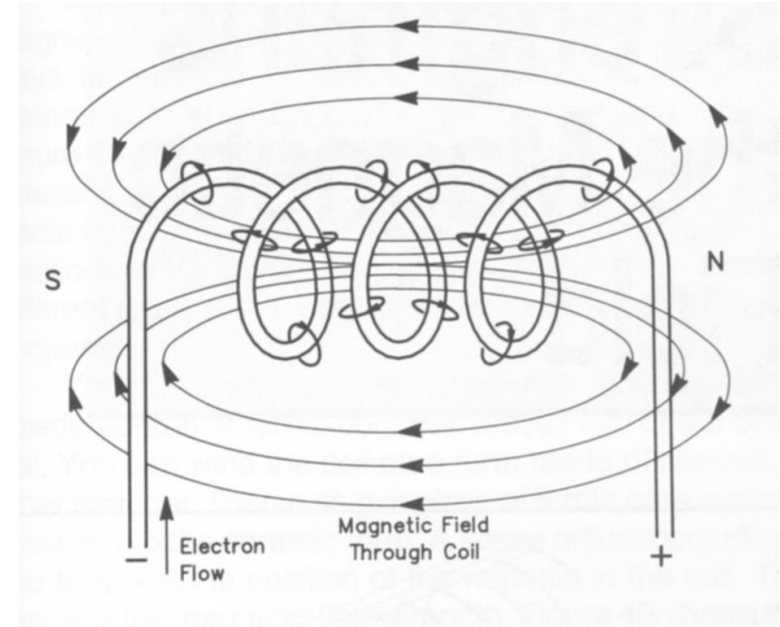- Like capacitors, inductors temporarily store energy
- Unlike capacitors:
  - Inductors store energy in a magnetic field, not an electric field
  - When the source of electrons is removed, the magnetic field collapses immediately



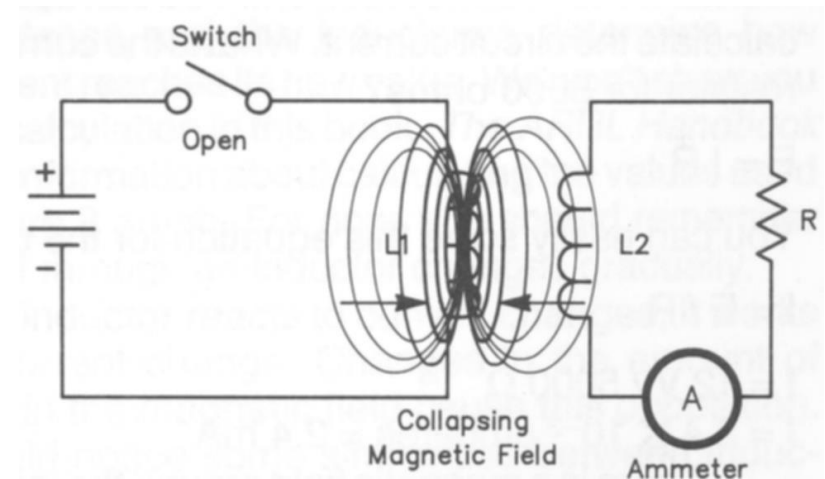
## Transformer

- Because the magnetic field surrounding an inductor can cut across another inductor in close proximity, the changing magnetic field in one can cause current to flow in the other.
- This is the basis of transformers



Inductance ( $L$ ) refers to the capacity of a coil to develop a voltage in it as the result of a changing magnetic flux. It is customary to use the symbol  $L$  for inductance, in honour of the physicist Heinrich **Lenz**.

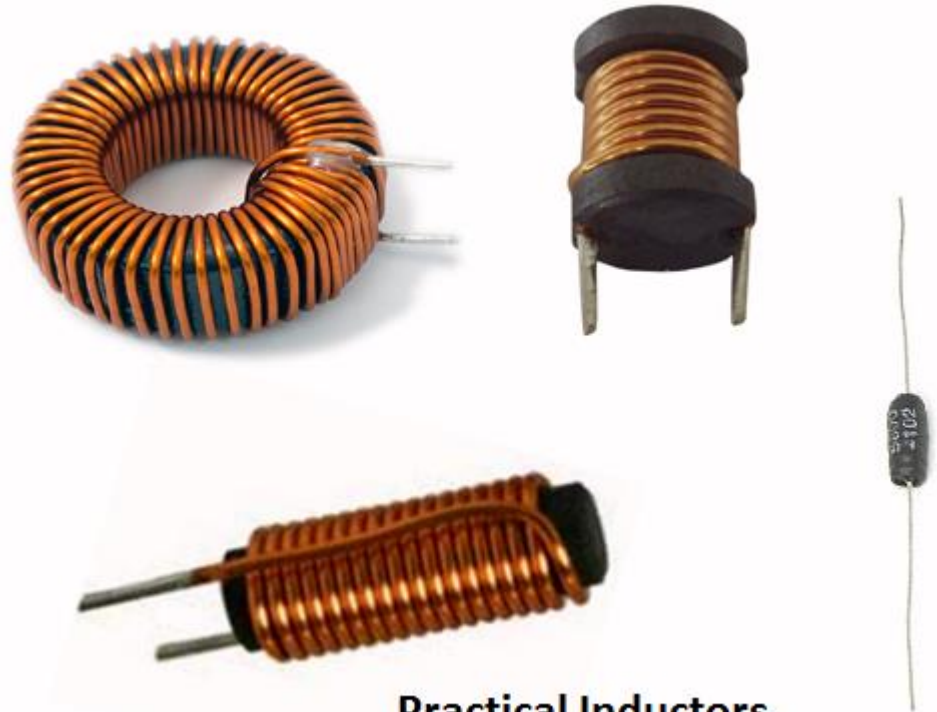In the metric system, the unit for inductance is the **henry ( $H$ )**, named in honor of Joseph Henry. The factors that determine the inductance include **the number of loops** of wire in the coil, the diameter or **area of the coil**, the **length of the coil** and the **permeability of the core material**.











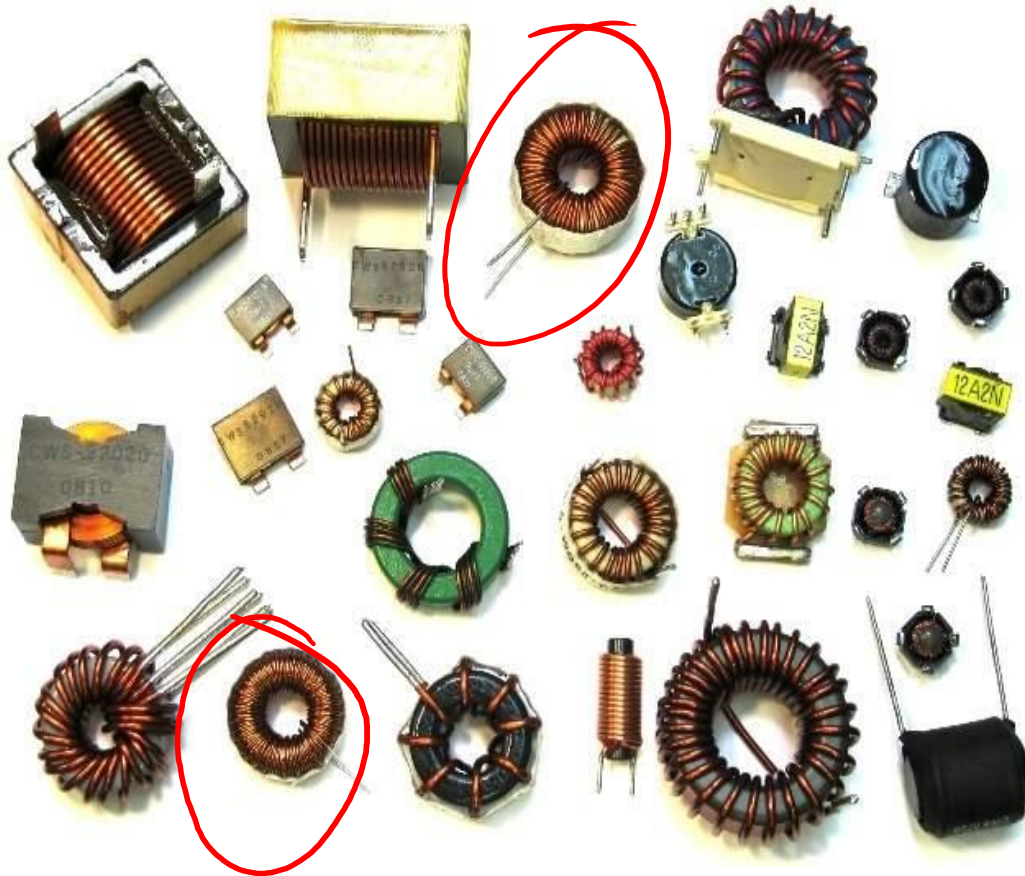

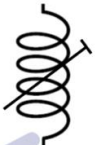
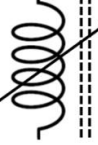

Practical Inductors
































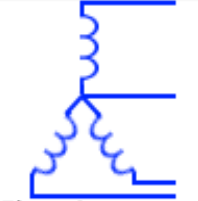
# Inductor




Inductor	Fixed	Variable	Pre-set	Shape
Air Core				
Iron Core				
Ferrite Core				



# Inductor Symbols

						
Inductor Generic US	FeSi Core inductor	Iron Core Inductor	Iron Core Inductor	Ferrite core inductor	Inductor with Polarity	Analog Delay Line
						
Variable Ferrite Core inductor	Preset Ferrite Core inductor	Continuous variation Inductor	Variable Ferrite Core inductor	Variable Inductor	Stepwise Variable Inductor	Stepwise Variable Inductor
						
Inductance	Inductor International	Inductance with power points	Shielded inductor	Electromagnet Solenoid	Electromagnet Solenoid	Electromagnetic deflection coil
						
Bifilar Inductor	Inductor with Fixed connections	Variometer	Saturable core inductor	Electromagnet	Preset Ferrite Core inductor	Electric motor inductors

- Inductors are simply coils of wire
  - Can be air wound (just air in the middle of the coil)
  - Can be wound around a permeable material (material that concentrates magnetic fields)
  - Can be wound around a circular form (toroid)
- The amount of inductance is influenced by a number of factors:
  - Number of coil turns
  - Diameter of coil
  - Spacing between turns
  - Size of the wire used
  - Type of material inside the coil

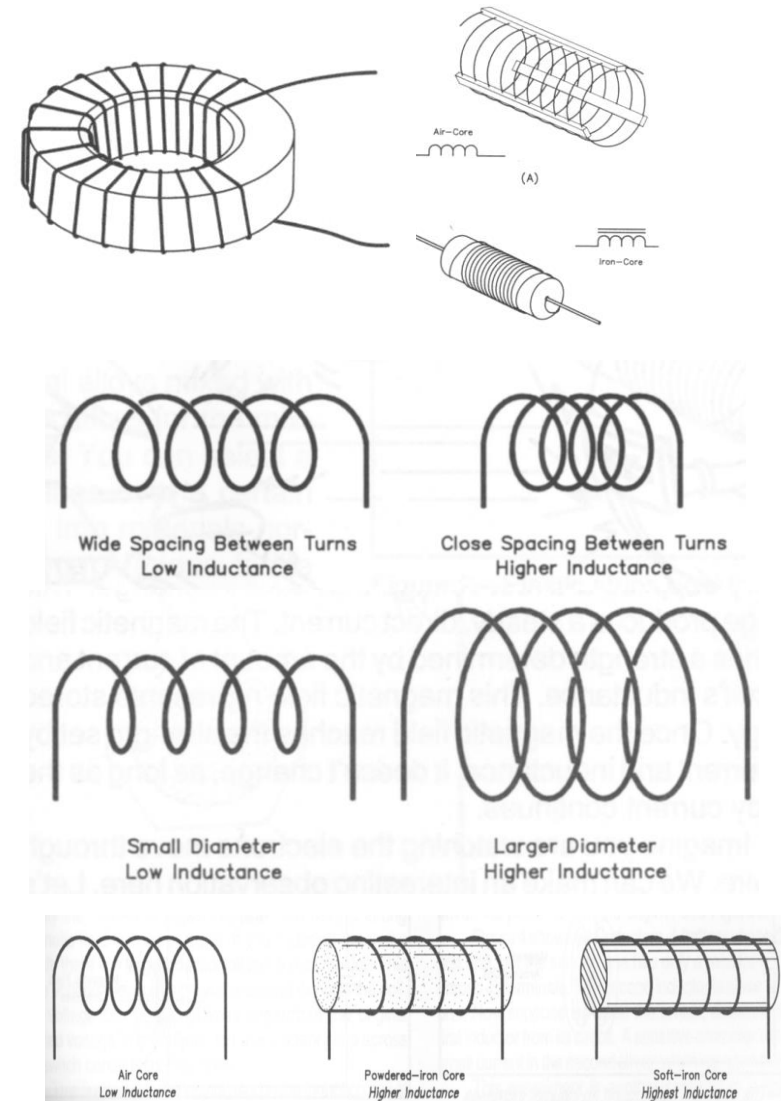


- When a DC current is first applied to an inductor, the increasing magnetic field opposes current flow - current flow is at a minimum
- Eventually (milliseconds) the magnetic field achieves its maximum and current flows, maintaining the field
- As soon as the current source is removed, the magnetic field begins to collapse and creates a rush of current in the other direction, sometimes at very high voltage

- When AC current is applied to an inductor, during the first half of the cycle, the magnetic field builds as if it were a DC current
- During the next half of the cycle, the current is reversed and the magnetic field decreases the reverse polarity in step with the changing current
- These forces can work against each other resulting in a lower current flow

An inductor is a passive element that stores energy in its magnetic field. Generally, An inductor consists of a coil of conducting wire wound around a core. For the inductor

$$v(t) = L \frac{di(t)}{dt}$$

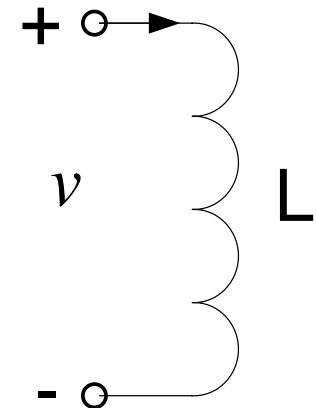where  $L$  is the inductance in henrys (H),  
and  $1 \text{ H} = 1 \text{ volt second/ampere}$ .




*Inductance is the property whereby an inductor exhibits opposition to the change of current flowing through it.*

# What happens in a wire?

Unfortunately, even bare wire has inductance.

$$L = \ell \left[ \ln \left( 4 \frac{\ell}{d} \right) - 1 \right] (2 \times 10^{-7}) H$$

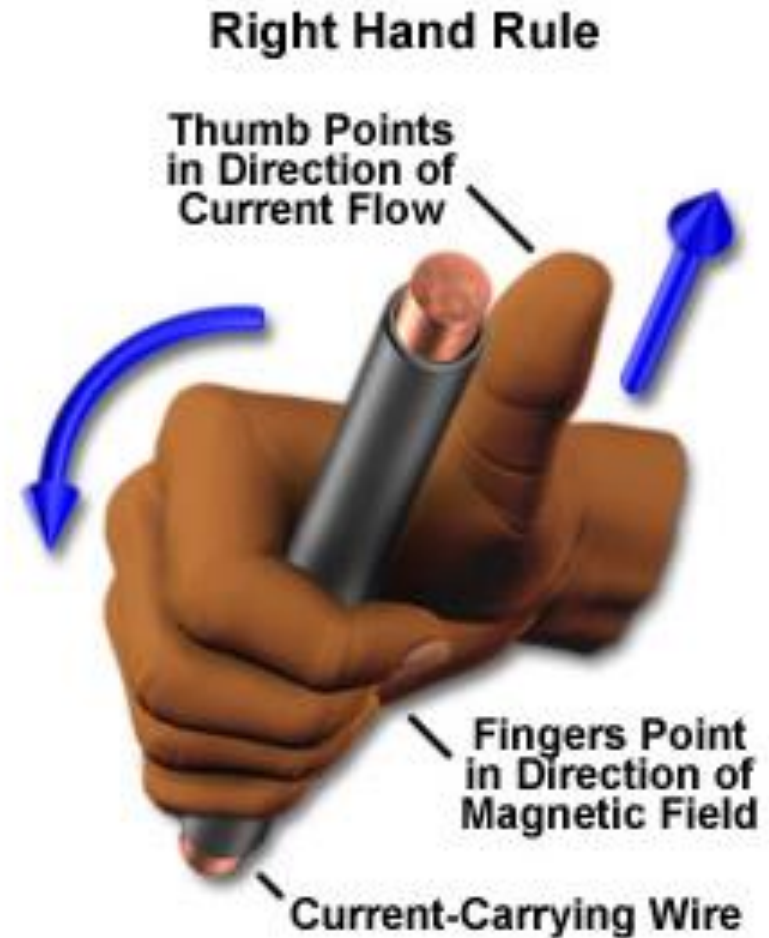$d$  is the diameter of the wire in meters.




# Material Inside Inductor

- For capacitors, we gained significantly by putting materials inside
- Can we gain any benefit by putting something in inductors?
- It gives you something to wrap around


Can materials increase the inductance?

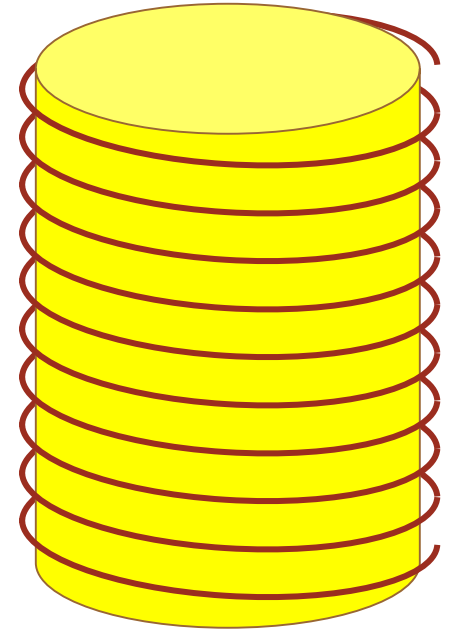- Most materials have negligible magnetic properties
- A few materials, like iron are *ferromagnetic*
  - They can enhance inductance enormously
- Many inductors (and similar devices, like transformers) have iron cores



Symbol for iron core inductor:


- We won't make this distinction

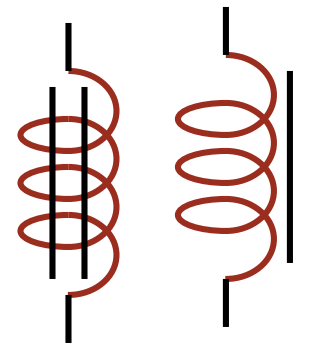


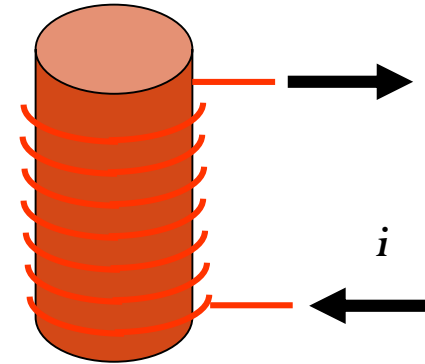
## Self-inductance of a solenoid

- Solenoid of cross-sectional area  $A$ , length  $l$ , total number of turns  $N$ , turns per unit length  $n$
- Field inside solenoid  $= \mu_0 n i$
- Field outside  $\sim 0$



$$\Phi_B = NAB = NA\mu_0 ni = Li$$

$$L = \text{“inductance”} = \mu_0 N A n = \mu_0 \frac{N^2}{l} A$$

Mutual Inductance of two coils:

Some of the magnetic flux through one coil also passes through the other coil, inducing a voltage.

Inductance is magnetic flux/current.

## Mutual inductance

The mutual inductance  $M$  of two coils is given by



$$M = M_{21} = M_{12} = \left| \frac{N_2 \Phi_{B2}}{i_1} \right| = \left| \frac{N_1 \Phi_{B1}}{i_2} \right|. \quad (21.11)$$

From the preceding analysis, we can also write

$$\mathcal{E}_2 = M \left| \frac{\Delta i_1}{\Delta t} \right| \quad \text{and} \quad \mathcal{E}_1 = M \left| \frac{\Delta i_2}{\Delta t} \right|. \quad (21.12)$$


Unit: The SI unit of mutual inductance is called the **henry** (1 H), in honor of Joseph Henry (1797–1878), one of the discoverers of electromagnetic induction. From Equation 21.11, one henry is equal to *one weber per ampere*. Other equivalent units, obtained by reference to Equation 21.10, are *one volt-second per ampere* and *one ohm-second*:
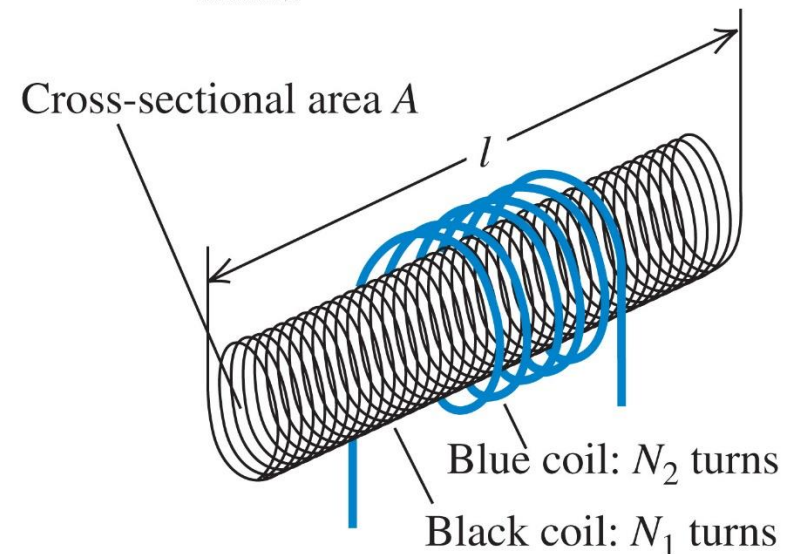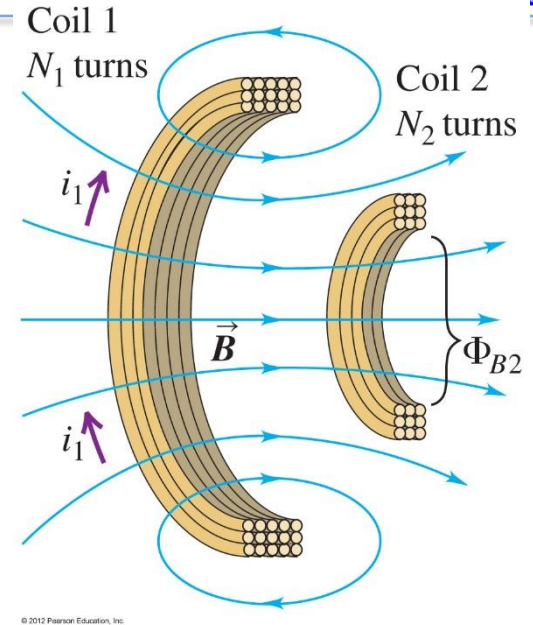
$$1 \text{ H} = 1 \text{ Wb/A} = 1 \text{ V} \cdot \text{s/A} = 1 \Omega \cdot \text{s}.$$


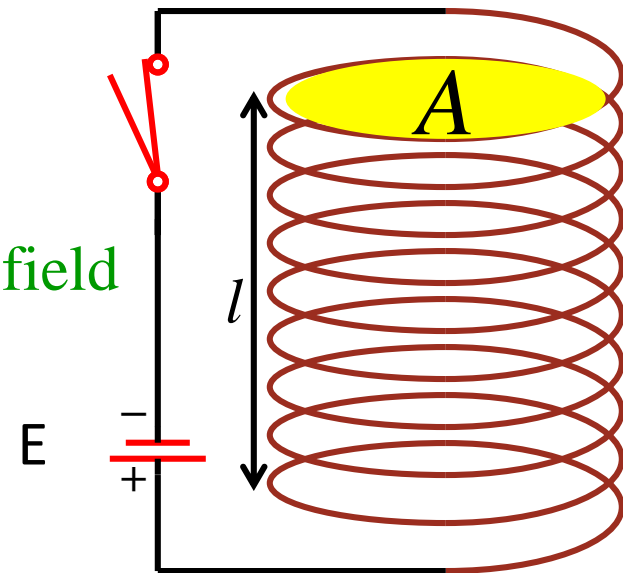
# Self Inductance

- Consider a solenoid  $L$ , connect it to a battery
  - Area  $A$ , length  $l$ ,  $N$  turns
- What happens as you close the switch?
- Lenz's law – loop resists change in magnetic field
- Magnetic field is caused by the current
- “Inductor” resists change in current



$$B = \frac{\mu_0 N I}{\ell} \quad \Phi_{B1} = \frac{\mu_0 N I A}{\ell}$$

$$E_L = -\frac{d\Phi_B}{dt} = -N \frac{d}{dt} \Phi_{B1} = -\frac{d}{dt} \left( \frac{\mu_0 N^2 I A}{\ell} \right) = -\frac{\mu_0 N^2 A}{\ell} \frac{dI}{dt}$$

$$E = -L \frac{dI}{dt}$$

$$L = \frac{\mu_0 N^2 A}{\ell}$$

Changing current through the wires in a coil will induce a voltage that opposes the **CHANGE** in the current.

## Definition of self-inductance

The self-inductance  $L$  of a circuit is the magnitude of the self-induced emf  $\mathcal{E}$  per unit rate of change of current, so that:

$$\mathcal{E} = L \left| \frac{\Delta i}{\Delta t} \right|. \quad (21.14)$$


From the definition, the units of self-inductance are the same as those of mutual inductance; the SI unit of self-inductance is *one henry*.

© 2012 Pearson Education, Inc.

## Energy Stored in an Inductor


$$U = \frac{1}{2} L I^2$$

SI unit: joule, J

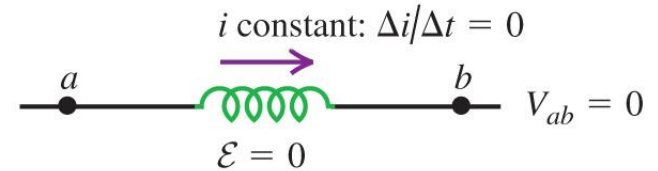


- (a) When the current is constant, there is no self-induced emf, so the voltage across the inductor is zero.

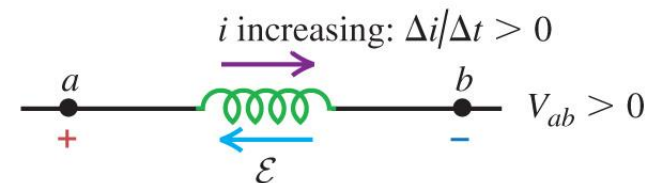(b) and (c) show that a changing current induces an emf and hence a voltage across the inductor.



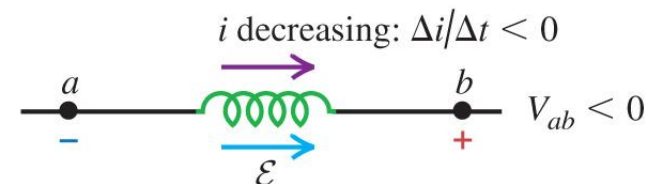- (b) If the current is *increasing*, then, by Lenz's law, the emf points opposite to  $i$ .




- (c) If the current is *decreasing*, then, by Lenz's law, the emf points in the same direction as  $i$ .

© 2012 Pearson Education, Inc.
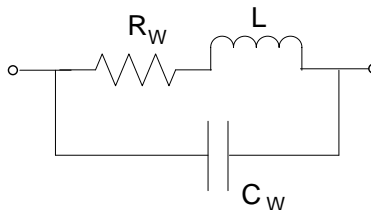
# Properties of Inductor

- An inductor acts like a short circuit to dc, since from ( $v = 0$  when  $i =$  a constant.)
$$v(t) = L \frac{di(t)}{dt}$$
- The current through an inductor cannot change **instantaneously**, since an instantaneous change in current would require an infinite voltage, which is not physically possible.
- Like the ideal capacitor, the ideal inductor does not dissipate energy.
- A real inductor has a significant resistance due to the resistance of the coil, as well as a “winding capacitance”. Thus, the model for a real inductor is shown below.



- If the current through an inductor is constant, the voltage across it is zero
- Thus, an inductor acts like a short for DC
- The current through an inductor cannot change instantaneously
- If this did happen, the voltage across the inductor would be infinity!
- This is an important consideration if an inductor is to be turned off abruptly; it will produce a high voltage

- Like the ideal capacitor, the ideal inductor does not dissipate energy stored in it.
- Energy stored will be returned to the circuit later
- In reality, inductors do have internal resistance due to the wiring used to make them.
- A real inductor thus has a winding resistance in series with it.
- There is also a small winding capacitance due to the closeness of the windings
- These two characteristics are typically small, though at high frequencies, the capacitance may matter.



- Voltage reaches its maximum right away
- **Current takes time to build up** as magnetic field is established

- Time constant for inductors is defined as:

- The time it takes the circuit to achieve 63% of the total expected current


- The time constant is calculated as:

$$T = \frac{L}{R} \quad \text{Values must be in base units (ie. H and } \Omega \text{)}$$



Where does the time constant value 63% come from?

$$\tau_n = 1 - e^{-n}$$

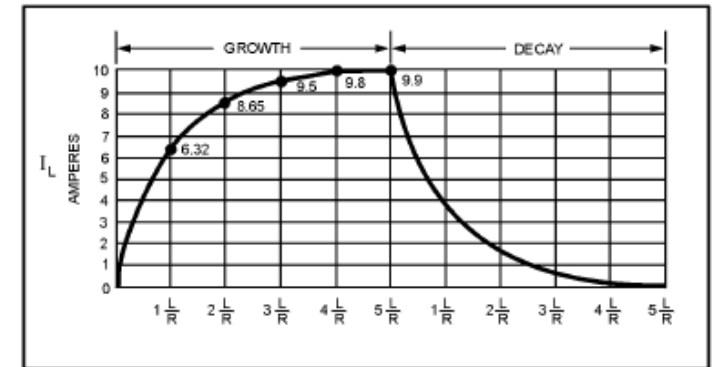63% of expected current after 1 time constant



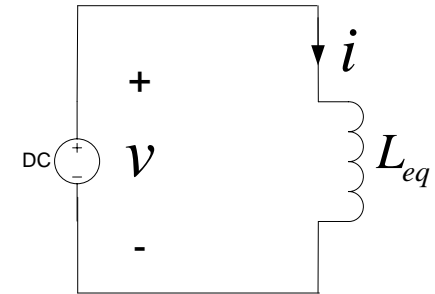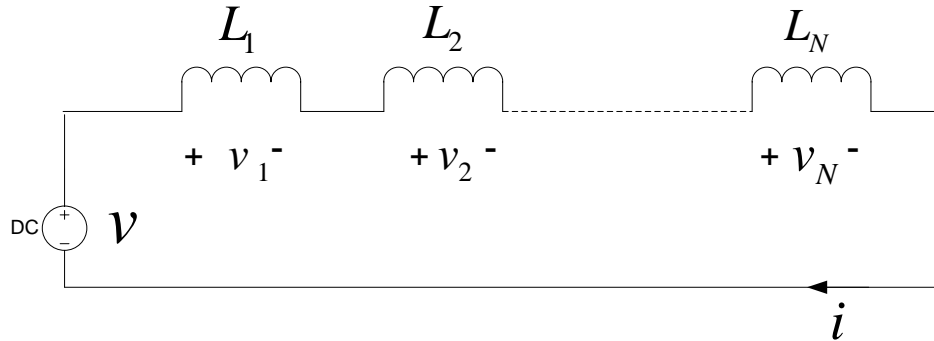It's built into the mathematics of exponential decay associated with first-order systems. If the response starts at unity at  $t=0$ , then after one "unit of time", the response is  $e^{-1}=0.36788$ . When you're looking at a risetime, you subtract this from unity, giving 0.63212 or 63.2%.



$$v_1 = L_1 \frac{di}{dt} \quad v_2 = L_2 \frac{di}{dt} \quad v_N = L_N \frac{di}{dt}$$

$$v = v_1 + v_2 + \dots + v_N = (L_1 + L_2 + \dots + L_N) \frac{di}{dt} = L_{eq} \frac{di}{dt}$$

$$L_{eq} = \sum_{k=1}^N L_k$$

***The equivalent inductance of series connected inductors is the sum of the individual inductances. Thus, inductances in series combine in the same way as resistors in series.***

- You have three inductors in series and their values are:

$$L_1 = 25\text{mH}$$

$$L_2 = 15\text{mH}$$


$$L_3 = 100\mu\text{H}$$



What is the total inductance of this simple circuit?

$$\begin{aligned} L_t &= L_1 + L_2 + \dots = L_1 + L_2 + L_3 \\ L_n &= 25\text{mH} + 15\text{mH} + 100\mu\text{H} \\ &= 40\text{mH} + 0.1\text{mH} \\ &= 40.1\text{mH} \end{aligned}$$

# Inductors in parallel

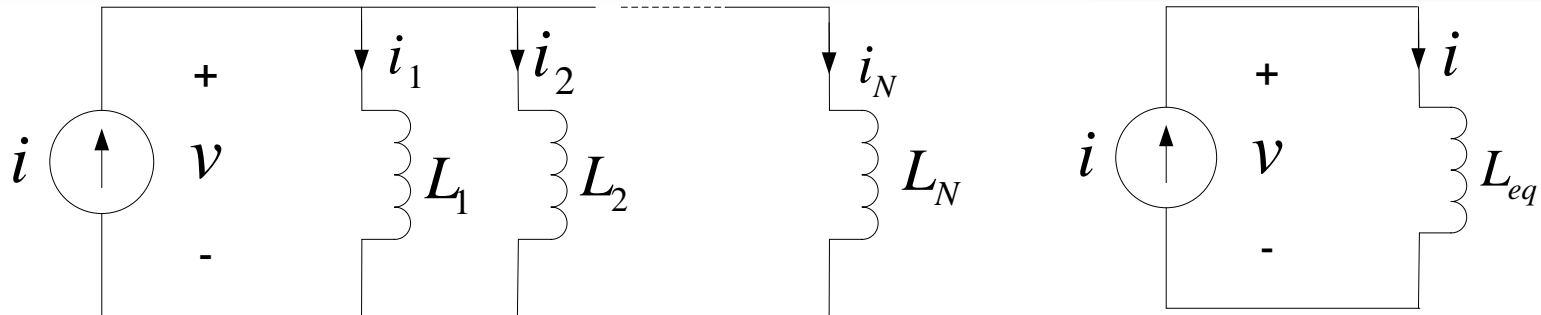

$$i_1 = \frac{1}{L_1} \int v dt$$

$$i_2 = \frac{1}{L_2} \int v dt$$

$$i_N = \frac{1}{L_N} \int v dt$$

$$i = i_1 + i_2 + \dots + i_N = \left( \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right) \int v dt = \frac{1}{L_{eq}} \int v dt$$

$$\frac{1}{L_{eq}} = \sum_{k=1}^N \frac{1}{L_k}$$

***The equivalent inductance of parallel connected inductors is the reciprocal of the sum of the reciprocals of the individual inductances.***


# Inductors in parallel: Example

- Now you have three inductors in parallel and their values are:

$$L_1 = 40\text{mH}$$

$$L_2 = 80\text{mH}$$

$$L_3 = 40\text{mH}$$

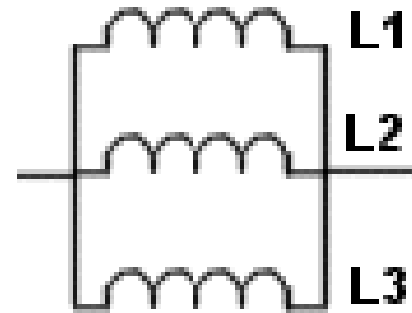



$$\frac{1}{L_t} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} = \frac{1}{40} + \frac{1}{80} + \frac{1}{40}$$

$$L_t = 16\text{mH}$$

A common pit-fall here is forgetting that the formula is based on  $1/L_t$   
Be sure that you recall this fact when you do the calculations on your own!

# INDUCTORS vs CAPACITORS

CAPACITOR	INDUCTOR
<p>Has a capacity to “hold” charge, called <b>capacitance</b>...</p> <p>[<math>C/V</math> = farad, F]</p> <p>...determined by its geometry:</p> $C = \frac{Q}{\Delta V}$ $C = \epsilon_0 \frac{A(N-1)}{d}$	<p>Has an ability to “hold” flux, called <b>inductance</b>...</p> <p>[<math>Wb/A = Tm/A</math> = henry, H]</p> <p>...determined by its geometry:</p> $L = \frac{\Phi_m}{I}$ $L = \mu_0 \frac{AN^2}{\ell}$
<p>Circuit diagram symbol:</p> 	<p>Circuit diagram symbol:</p> 
<p>Stores energy in its electric field:</p> $U_C = \frac{1}{2} C (\Delta V)^2$ $u_E = \frac{\epsilon_0}{2} E^2$	<p>Stores energy in its magnetic field:</p> $U_L = \frac{1}{2} L I^2$ $u_B = \frac{1}{2\mu_0} B^2$
<p>Regulates current through a series resistor...</p>	
<p>...at switch on:</p> $I = \frac{E}{R} e^{-t/\tau}$	<p>...at switch on:</p> $I = \frac{E}{R} (1 - e^{-t/\tau_L})$
<p>...and switch off:</p> $I = I_0 e^{-t/\tau}$	<p>...and switch off:</p> $I = I_0 e^{-t/\tau_L}$