
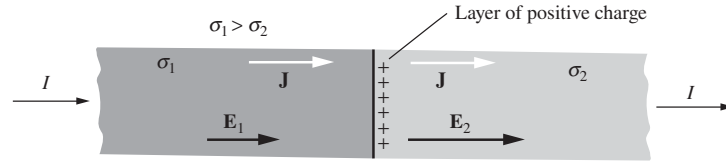

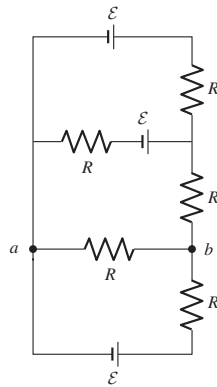
## PHY102 : Assignment 5


- (P&M 4.2) Show that the total amount of charge at the junction of two materials as shown, is  $I\epsilon_0(1/\sigma_1 - 1/\sigma_2)$ , where  $I$  is the current flowing through the junction and  $\sigma_1$  and  $\sigma_2$  are the conductivities of the two conductors.




- (P&M 4.12) What is the potential difference between points a and b in the circuit shown in Fig. ?



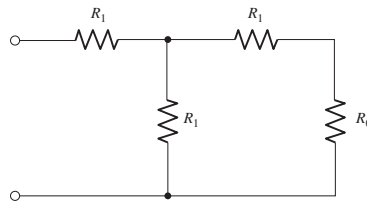
- (P&M 4.29) In the circuit, if  $R_0$  is given, what value must  $R_1$  have in order that the input resistance between the terminals should be equal to  $R_0$  ?



- (P&M 4.31) A black box with three terminals,  $a, b, c$  contains nothing but three resistors and connecting wire. Measuring the resistance between pairs of terminals, we find  $R_{ab} = 30$  ohms,  $R_{ac} = 60$  ohms and  $R_{bc} = 70$  ohms. Show that the contents of the box could be either configuration as shown in figure. Is there any other possibility ? Are the two boxes completely equivalent, or is there an external measurement that would distinguish between them ?

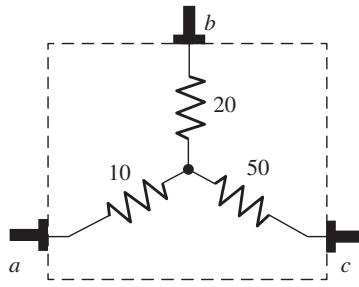

or

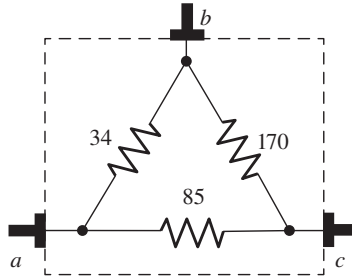

5. (P&M 4.35) A cube has a resistor  $R$  along each edge. Find the equivalent resistance between two nodes that correspond to:

- diagonally opposite corners of the cube;
- diagonally opposite corners of a face;
- adjacent corners.

You do not need to solve a number of simultaneous equations; instead use symmetry arguments. Hint: If two vertices are at the same potential, they can be collapsed to one point without changing the equivalent resistance between the two given nodes.